

PHYSICS CIRCUITS STUDY GUIDE

Name: Key

Equations

$$\Delta V = IR$$

$$R_{eg} = R_1 + R_2 + \dots + R_n$$

$$\frac{1}{R_{eg}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}$$

Things you should be able to do / know / understand!

- Use Ohm's Law to calculate potential difference across a resistor, current through a resistor, or the value of a resistor.
- Use power and its different "flavors" to solve problems
 - o Knowing which equation of power to use when solving conceptual problems.
- Identify the type of circuit (series/parallel)
- Find total resistance in a circuit (series and parallel)
- Know the properties of a series and parallel circuit
- Use the properties of a series and parallel circuit to solve for unknown quantities
- Know how to use a voltmeter and ammeter to measure voltage and current respectively in a circuit

Problems

1. For each term, write a brief definition, write its variable and the unit that it is measured in.

Term	Variable	Measuring Unit	Definition
Current	I	Amps, A	flow of electricity (electrons)
Voltage	V	Voltage, V	Potential Energy of circuits
Resistance	R	Ohms, Ω	Uses electricity, slows the flow

2. What is the equation for Ohm's Law? What is the relationship between voltage, current, and resistance?

$$V = IR$$

If... $V \uparrow$ then $I \uparrow$; $I \uparrow$ then $R \downarrow$
 $V \uparrow$ then $R \uparrow$

3. If 0.2 A of current is drawn by a lamp when a voltage of 12 V is used, what is the resistance?

$$\frac{12V}{0.2A} = \frac{0.2A R}{0.2A}$$

$R = 60 \Omega$

4. What is the resistance of an electric frying pan that draws 12 A when connected to a 120 V circuit?

$$\frac{120V}{12A} = \frac{12A R}{12A}$$

$R = 10 \Omega$

5. At a resistance of 100,000 Ω , what will be the current in your body if you touch the terminals of a 12-volt battery?

$$\frac{12V}{100,000 \Omega} = \frac{I (100,000 \Omega)}{100,000 \Omega}$$

$I = 1.2 \times 10^{-4} \text{ Amps}$

Circuit Basics -

6. What is the schematic symbol for a battery?




7. What is the schematic symbol for a resistor or a lightbulb?



$V = 0.1 (10)$

8. Fill out the table for the circuit diagramed at the right.

Circuit Position	Voltage (V)	Current (A)	Resistance (Ω)
$V=IR \rightarrow$ 1	1V	0.1A	10.0
$V=IR \rightarrow$ 2	2V	0.1A	20.0
$V=IR \rightarrow$ 3	3V	0.1A	30.0
$V=IR \rightarrow$ Battery	6.00	0.1A	60 Ω

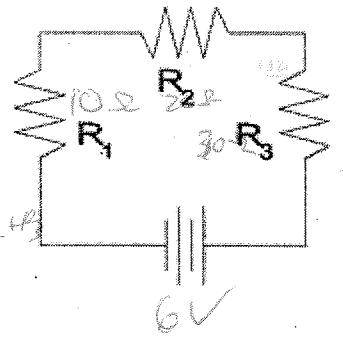

$R_{tot} = R_1 + R_2 + R_3$

$60V = I \cdot 60\Omega$


Which of the lightbulb would be the brightest?

Bulb 3 \rightarrow highest Voltage and same currents

$(6) = I (10)$

9. Fill out the table for the circuit diagramed at the right.

Circuit Position	Voltage (V)	Current (A)	Resistance (Ω)
$V=IR \rightarrow$ 1	6V	0.6A	10.0
$V=IR \rightarrow$ 2	6V	0.3A	20.0
$V=IR \rightarrow$ 3	6V	0.2A	30.0
$V=IR \rightarrow$ Battery	6.00	1.1A	5.45 Ω

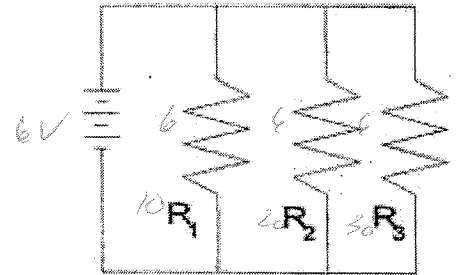

$I_{tot} = I_1 + I_2 + I_3$

Which of the lightbulb would be the brightest?

$6 = 1.1 R$


Bulb 1 - same Voltage, higher current.

Questions 10 and 11 refer to the following:

The diagram to the right represents an electric circuit consisting of four resistors and a 12-volt battery.

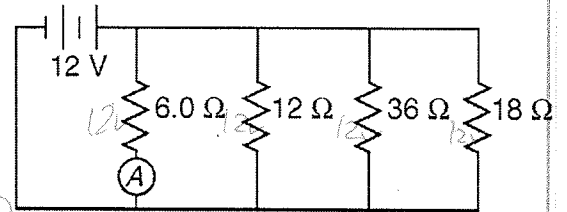10. What is the equivalent resistance of the circuit shown?

$\frac{1}{R_{tot}} = \frac{1}{6} + \frac{1}{12} + \frac{1}{36} + \frac{1}{18} = \frac{1}{3}$ $R_{tot} = 3\Omega$




11. What is the current measured by ammeter A shown in the diagram?

$V=IR$ $\frac{12}{6} = \frac{I(6)}{6}$ $I = 2 \text{ Amps}$

12. A circuit with a 50.0-V battery consists of a series combination of two lamps with resistances of 125 Ω and 225 Ω .

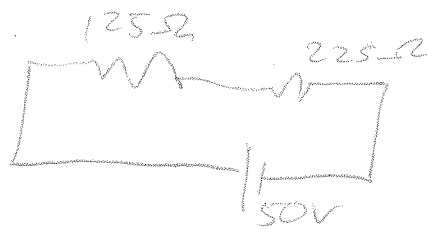a. Draw the circuit and calculate all values.



b. What is the total resistance of the circuit?

350Ω

c. What is the current in the circuit?

$125 + 225 = 350$


d. What is the voltage across the 125- Ω lamp?

$\frac{50}{350} = \frac{I(125)}{350}$ $I = 0.14 \text{ amps}$

$V=IR$
 $(0.14)(125) = 17.5V$

13. A circuit with a 12-V battery consists of a series combination of three resistances are $15\ \Omega$, $21\ \Omega$, and $24\ \Omega$, respectively.

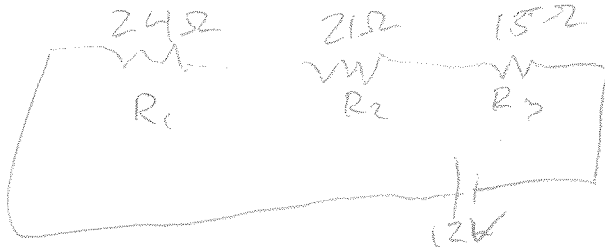a. Draw the circuit and calculate all values.



	V	I	R
R_1	4.8V	0.2A	$24\ \Omega$
R_2	4.2V	0.2A	$21\ \Omega$
R_3	3V	0.2A	$15\ \Omega$
Tot	12V	0.2A	$60\ \Omega$

b. What is the total resistance of the circuit?

$$24 + 21 + 15 = 60\ \Omega$$

c. What is the magnitude of the circuit current?


$$12 = I \cdot 60 \quad I = 0.2\text{A}$$

d. If the resistors were lightbulbs, which would be the brightest? Which would be the dimmest?

$R_1 = \text{Brightest (highest V)}$ $R_3 = \text{Dimmest (lowest V)}$

14. A circuit with a 40-V battery consists of a series combination of three resistances R_1 , R_2 , and R_3 . R_1 is $240\ \Omega$, and R_3 is $120\ \Omega$. The voltage across R_1 is 24 V.

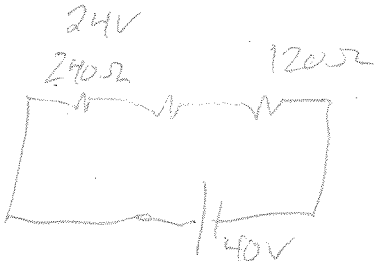a. Draw the circuit and calculate all values.



	V	I	R
R_1	24V	0.1V	$240\ \Omega$
R_2	4V	0.1V	$40\ \Omega$
R_3	12V	0.1V	$120\ \Omega$
tot	40V	0.1V	$400\ \Omega$

b. Find the current in the circuit.

$$24 = I \cdot 240$$

c. Find the equivalent resistance of the circuit.


$$400 - 120 - 240 = 40\ \Omega$$

d. Find the resistance of R_2 .

$$40 = 0.1 R$$

15. The load across a 12-V battery consists of a series combination of three resistances R_1 , R_2 , and R_3 . R_1 is $210\ \Omega$, R_2 is $350\ \Omega$, and R_3 is $120\ \Omega$.

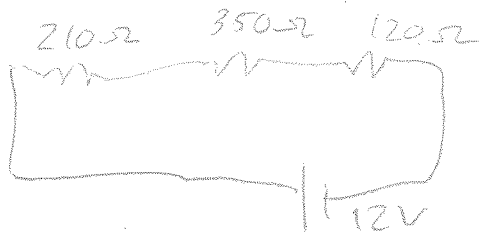a. Draw the circuit and calculate all values.



	V	I	R
R_1	2.57V	0.017A	$210\ \Omega$
R_2	5.97	0.017	$350\ \Omega$
R_3	2.11V	0.017	$120\ \Omega$
tot	12V	0.017A	$680\ \Omega$

b. What is the equivalent resistance of the circuit?

$$210 + 350 + 120 = 680$$

c. What is the current in the circuit?

$$12 = I \cdot 680$$

d. What is the voltage across R_3 ?

$$V = (0.017)(120)$$

16. 18. Two resistances, one $12\ \Omega$ and the other $18\ \Omega$, are connected in parallel. What is the equivalent resistance of the parallel combination?


$$\frac{1}{12} + \frac{1}{18} = \frac{1}{R_{tot}} = \frac{5}{36} \quad \text{flip} \quad R_{tot} = \frac{36}{5}\ \Omega$$

17. Three resistances of $12\ \Omega$ each are connected in parallel. What is the equivalent resistance?

$$\frac{1}{12} + \frac{1}{12} + \frac{1}{12} = \frac{1}{R_{tot}} = \frac{3}{12} \quad R_{tot} = \frac{12}{3} = 4\ \Omega$$

18. Two resistances, one $62\ \Omega$ and the other $88\ \Omega$, are connected in parallel. The resistors are then connected to a 12-V battery.

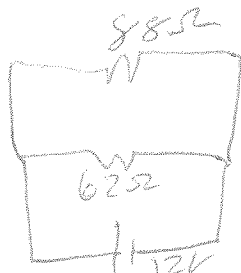- a. Draw the circuit and calculate all values.



	V	I	R
R_1	12V	0.193A	$62\ \Omega$
R_2	12V	0.136A	$88\ \Omega$
tot	12V	0.329A	$36.475\ \Omega$

- b. What is the equivalent resistance of the parallel combination?

$$\frac{1}{62} + \frac{1}{88} = \frac{1}{R_{tot}} \quad \text{flip}$$

- c. What is the current through the $62\ \Omega$ resistor?

$$12 = I(62) = 0.193\ \text{A}$$

- d. What is the current through the $88\ \Omega$ resistor?

$$12 = I(88) = 0.136\ \text{A}$$

19. A $35\text{-}\Omega$, $55\text{-}\Omega$, and $85\text{-}\Omega$ resistor are connected in parallel. The resistors are then connected to a 35-V battery.

- a. Draw the circuit and calculate all values.



	V	I	R
R_1	35V	1A	$35\ \Omega$
R_2	35V	0.63A	$55\ \Omega$
R_3	35V	0.41A	$85\ \Omega$
Tot	35V	2.04A	$17.15\ \Omega$

- b. What is the equivalent resistance of the parallel combination?

$$\frac{1}{35} + \frac{1}{55} + \frac{1}{85} = \frac{1}{R_{tot}} \quad \text{flip}$$

- c. What is the current through the $35\text{-}\Omega$ resistor?

$$35 = I(35)$$

- d. What is the current through the $55\text{-}\Omega$ resistor?

$$35 = I(55)$$

- e. What is the current through the $85\text{-}\Omega$ resistor?

$$35 = I(85)$$

- f. If the resistors were lightbulbs, which would be the brightest? Which would be the dimmest?

$35\ \Omega$ = brightest (higher current)

$85\ \Omega$ = Dimmest (lowest current)